



Fermilab

*Noise
In
RF Systems*

Ralph J. Pasquinelli




Fermilab

Noise in RF Systems

What are sources of electrical noise?

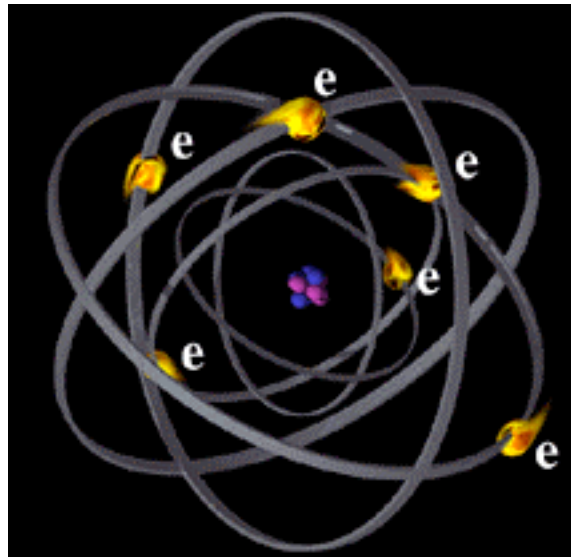*Random motion of electrons produces thermal noise
Sometimes referred to as “white noise”*






Fermilab


Noise in RF Systems

What are sources of electrical noise?

Vacuum Tube

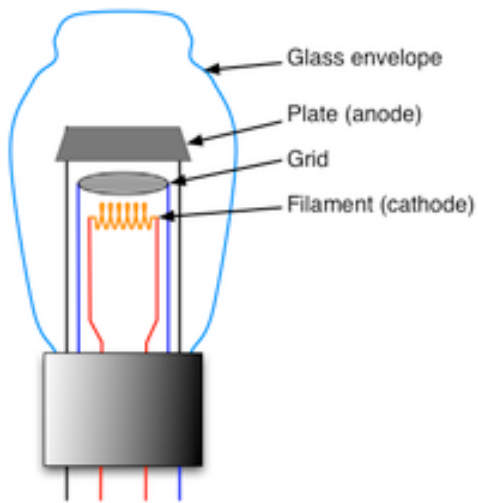

Transistor

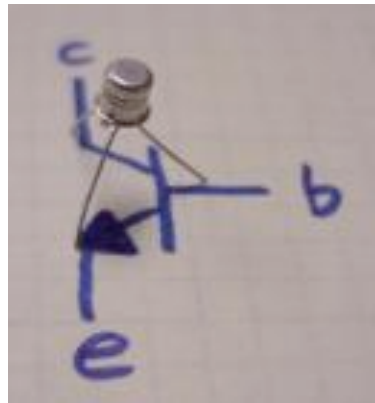

Particle Accelerator



R. J. Pasquinelli




Fermilab

Noise in RF Systems

What are sources of electrical noise?

Other undesirable charged particles

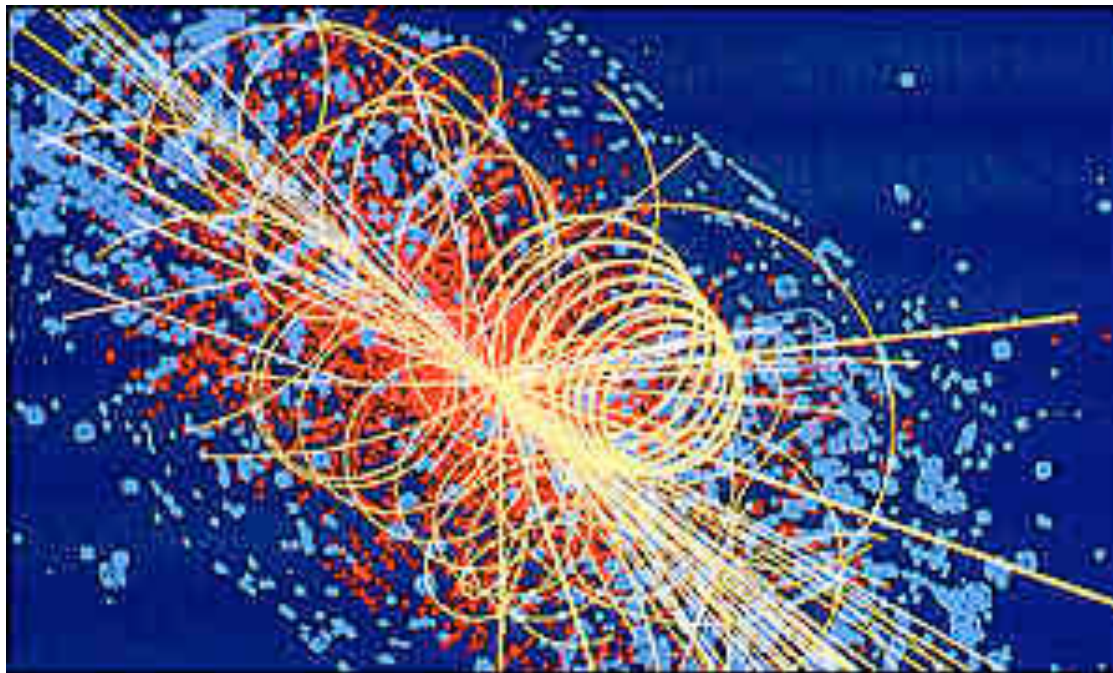

R. J. Pasquinelli



Fermilab

Noise in RF Systems


Noise Basics



Thermal Noise = kTB

Boltsman's constant x Temperature x Bandwidth
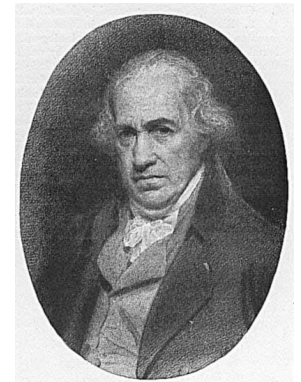
$$\frac{\text{Watt Seconds}}{\text{Degrees K}} \times \text{Degrees K} \times \frac{1}{\text{Seconds}}$$



R. J. Pasquinelli




Fermilab

Noise in RF Systems

Noise Basics

Noise unit is watts

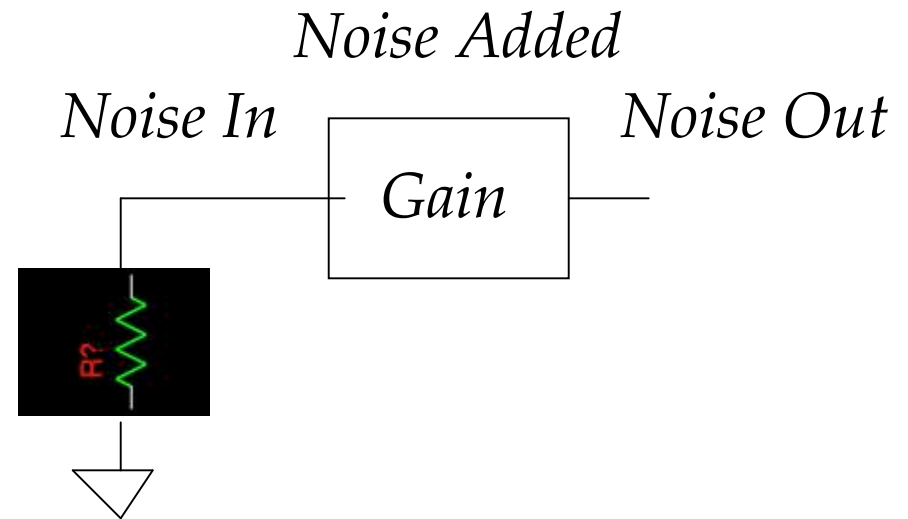

$$\begin{aligned}
 \text{Noise Figure} & \text{ or } \text{Noise Factor} = NF = \frac{\frac{\text{Signal In}}{\text{Noise In}}}{\frac{\text{Signal Out}}{\text{Noise Out}}} = \frac{\cancel{(\text{Signal In})}(\text{Noise Out})}{(\text{Gain})(\cancel{\text{Signal In}})(\text{Noise In})} = \frac{\text{Noise Out}}{(\text{Gain})(\text{Noise In})}
 \end{aligned}$$


The Perfect Gain Box adds no noise, so NF=1 or 0 dB



Fermilab

Noise in RF Systems

Noise Basics

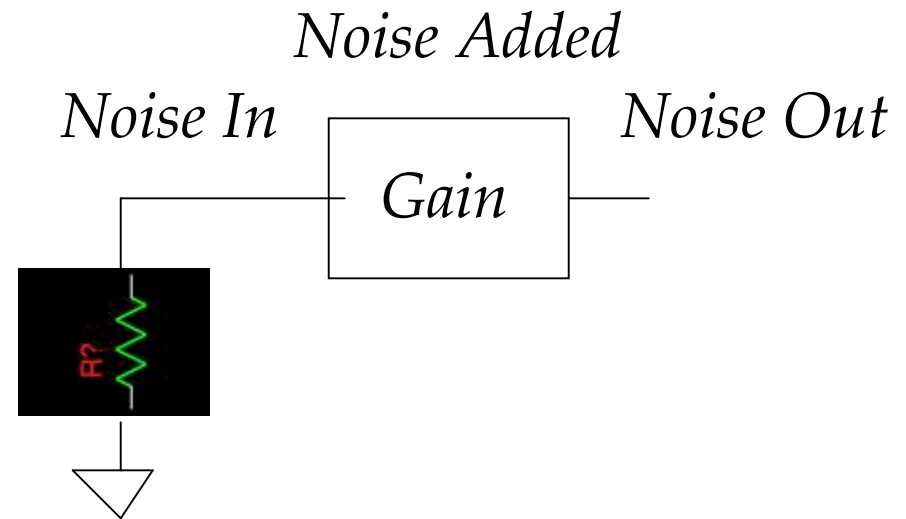

$$\text{Noise Out} = \text{Noise In} \times \text{Gain} + \text{Noise Added}$$

$$\begin{aligned}\text{Noise Added} &= \text{Noise Out} - \text{Noise In} \times \text{Gain} \\ &= NF \times \text{Noise In} \times \text{Gain} - \text{Noise In} \times \text{Gain} \\ &= (NF - 1) \times \text{Noise In} \times \text{Gain}\end{aligned}$$

$$\text{Noise In} = kTB$$



Fermilab

Noise in RF Systems

Noise Basics

Where is the noise floor?

Temperature Dependent

Noise Energy = kT = joules = watt seconds


$$=(1.38 \times 10^{-23} \text{ joules/K}) \times (290 \text{ K})$$

$$=4 \times 10^{-21} \text{ joules}$$

$$=4 \times 10^{-18} \text{ milliwatt seconds}$$

$$=-174 \text{ dBm per Hz}$$

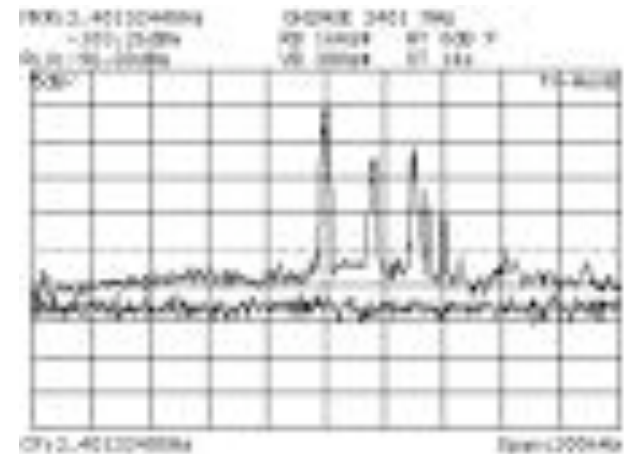Have a MHz of Bandwidth then add 60 dB for -114 dBm per MHz






Fermilab

Noise in RF Systems

Noise Basics

How to Measure Noise Figure

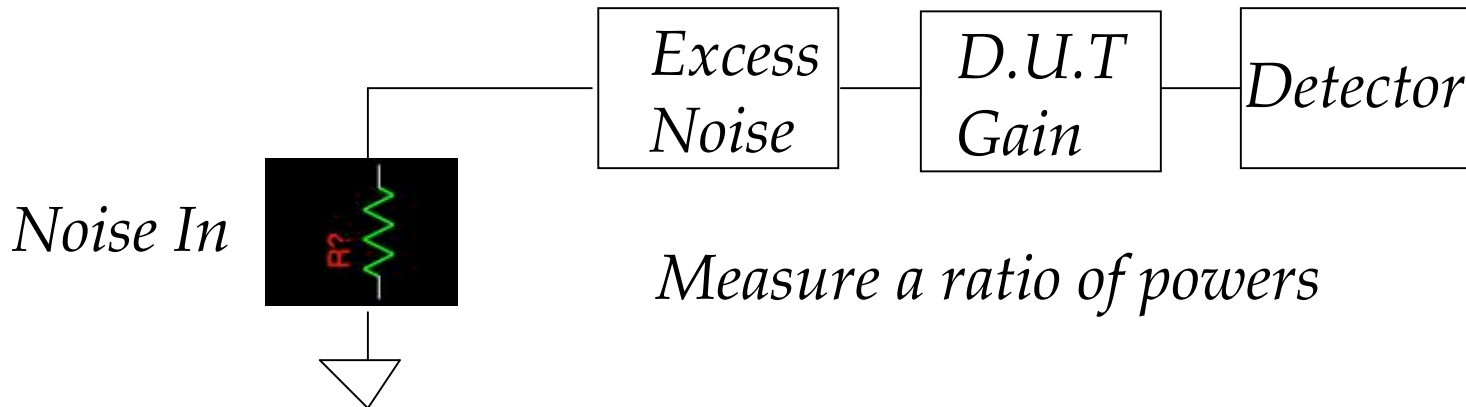

Measure a ratio of powers

excess noise on

<i>Excess Noise x Gain</i>

<i>D.U.T added Noise</i>

<i>Noise In x Gain</i>

excess noise off

<i>D.U.T added Noise</i>

<i>Noise In x Gain</i>




Fermilab

Noise in RF Systems

Noise Basics

How to Measure Noise Figure

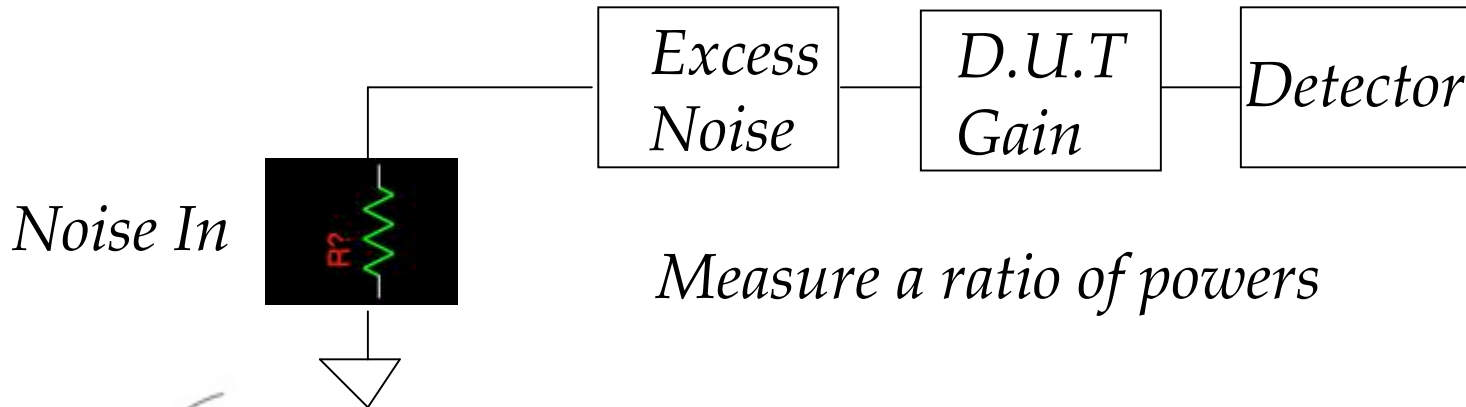

Measure a ratio of powers



$$NF = \text{Excess Noise Ratio} \times \frac{1}{\text{Measured Ratio} - 1}$$




Fermilab

Noise in RF Systems

Noise Basics

How to Measure Noise Figure

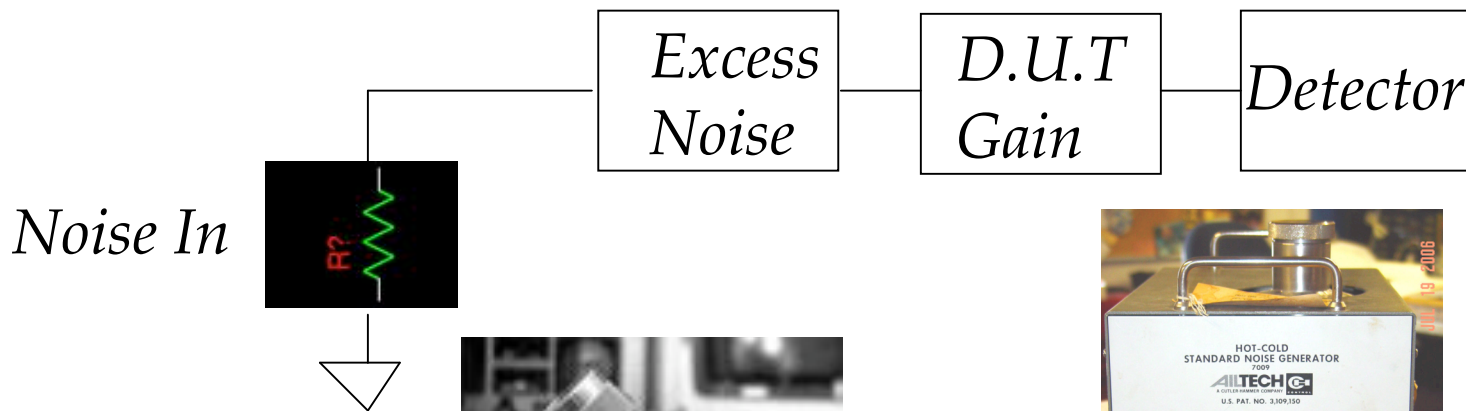

Noise Diode



Hot and Cold noise source


R. J. Pasquinelli



Fermilab

Noise in RF Systems

Noise Figure Test Setup

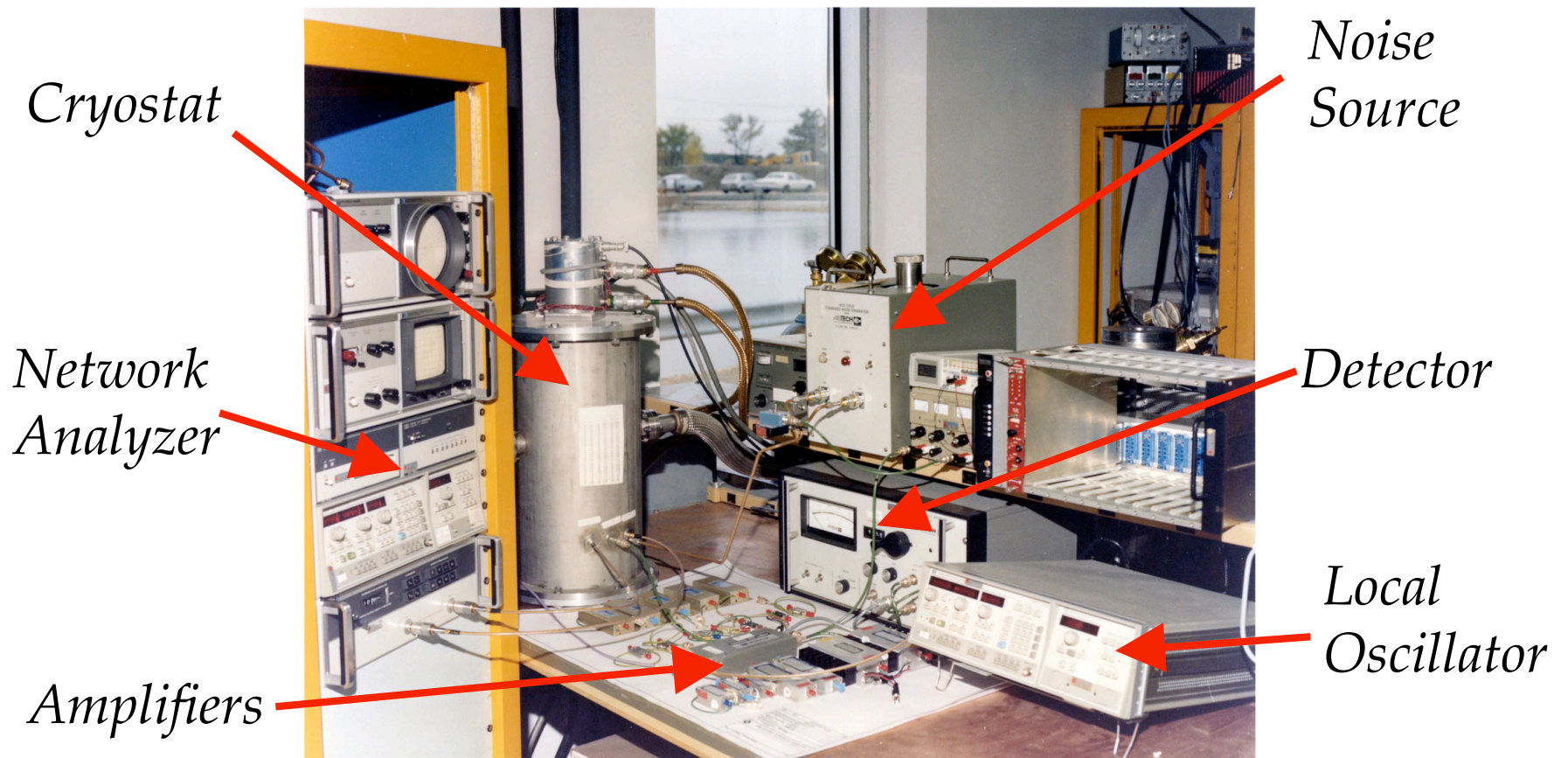

R. J. Pasquinelli




Fermilab

Noise in RF Systems

Noise Basics

System Noise Figure

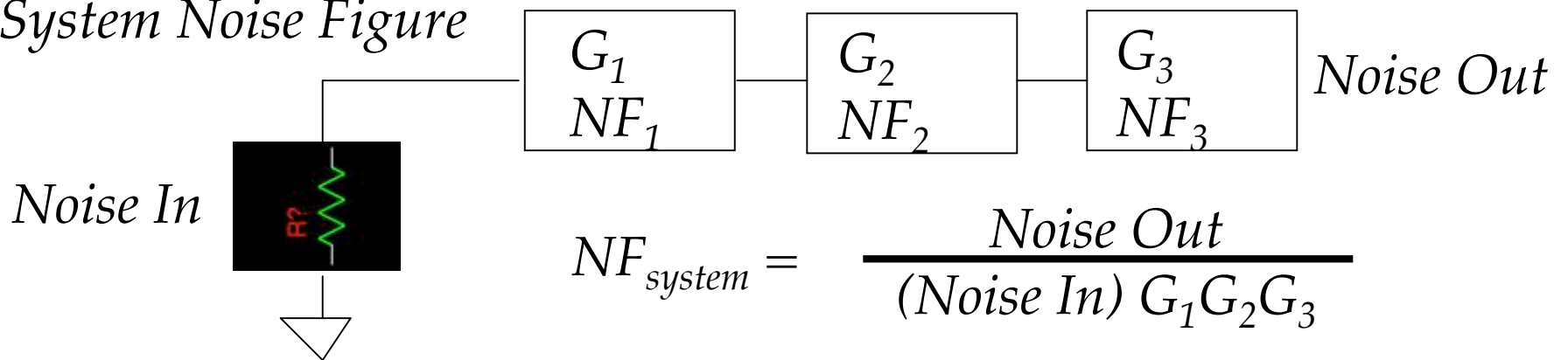

$$NF_{system} = \frac{\text{Noise Out}}{(\text{Noise In}) G_1 G_2 G_3}$$

$$NF_{system} = \frac{\cancel{kTBG_1G_2G_3} + (NF_1-1)\cancel{kTBG_1G_2G_3}}{\cancel{kTBG_1G_2G_3}} + \frac{(NF_2-1)\cancel{kTBG_2G_3}}{\cancel{kTBG_1G_2G_3}} + \frac{(NF_3-1)\cancel{kTBG_3}}{\cancel{kTBG_1G_2G_3}}$$

$$NF_{system} = NF_1 + \frac{NF_2 - 1}{G_1} + \frac{NF_3 - 1}{G_1 G_2}$$

R. J. Pasquinelli



Fermilab

Noise in RF Systems


***Mount Amplifier
HERE!***





Fermilab

Noise in RF Systems

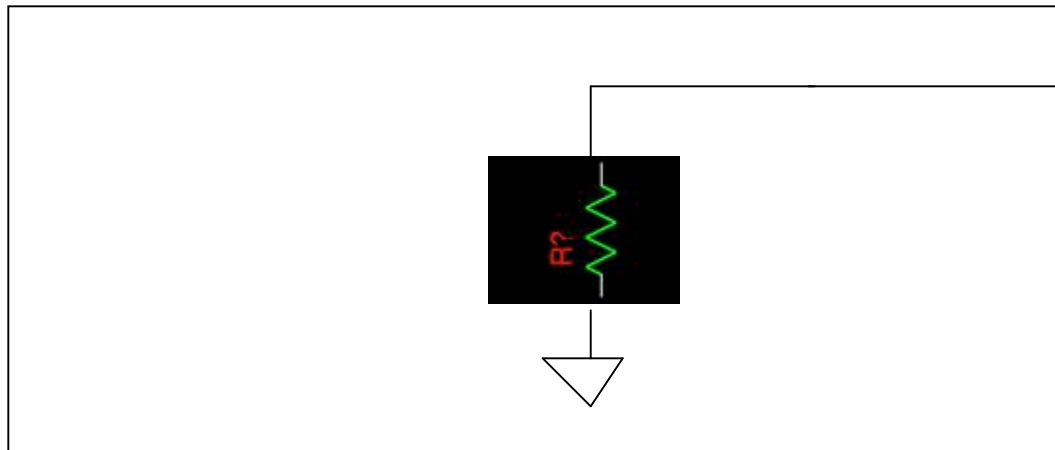

*Look into these boxes
The impedance
looks the same!*


R. J. Pasquinelli



Fermilab

Noise in RF Systems

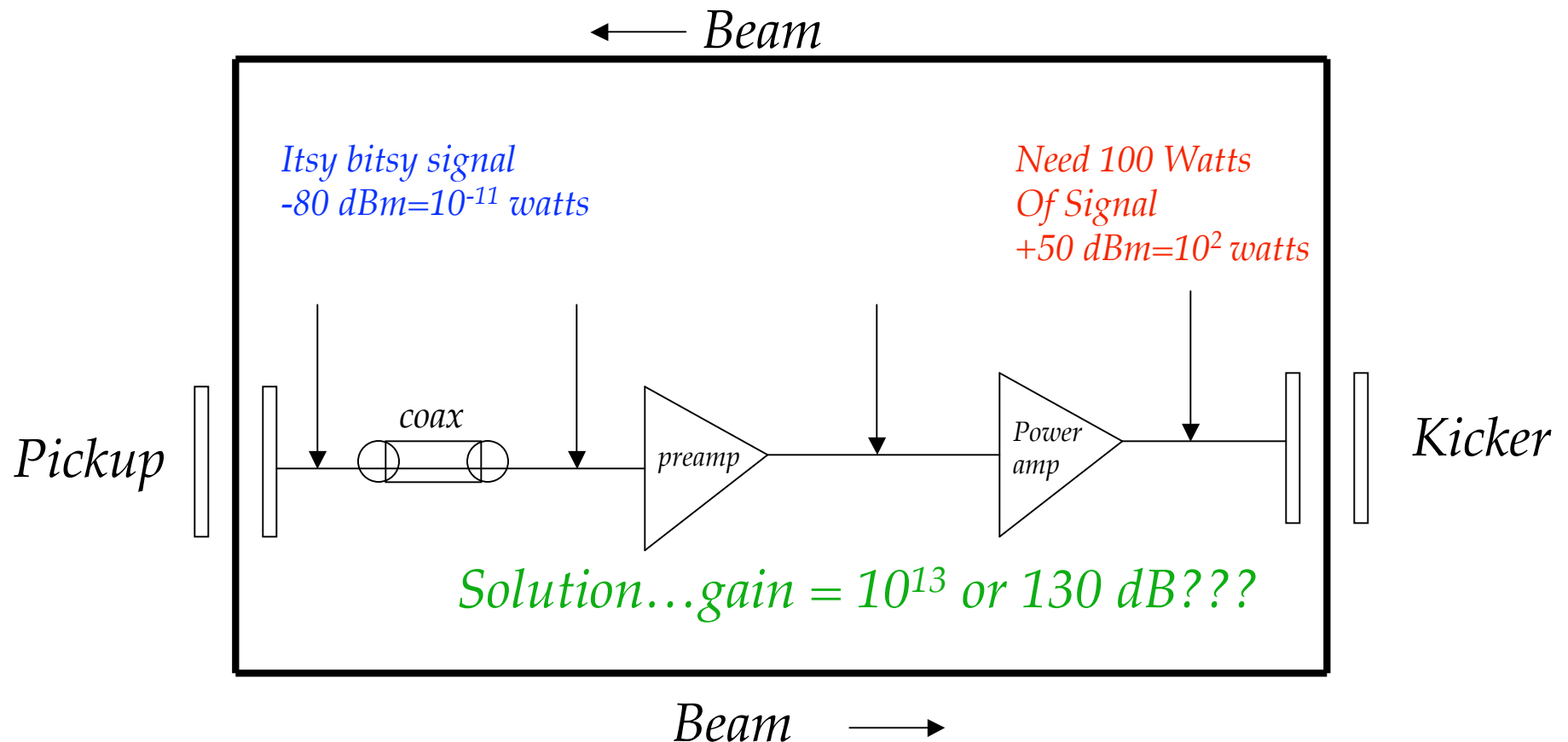Typical Stochastic Cooling Feedback System






Fermilab

Noise in RF Systems

Typical Stochastic Cooling Feedback System

← *Beam*

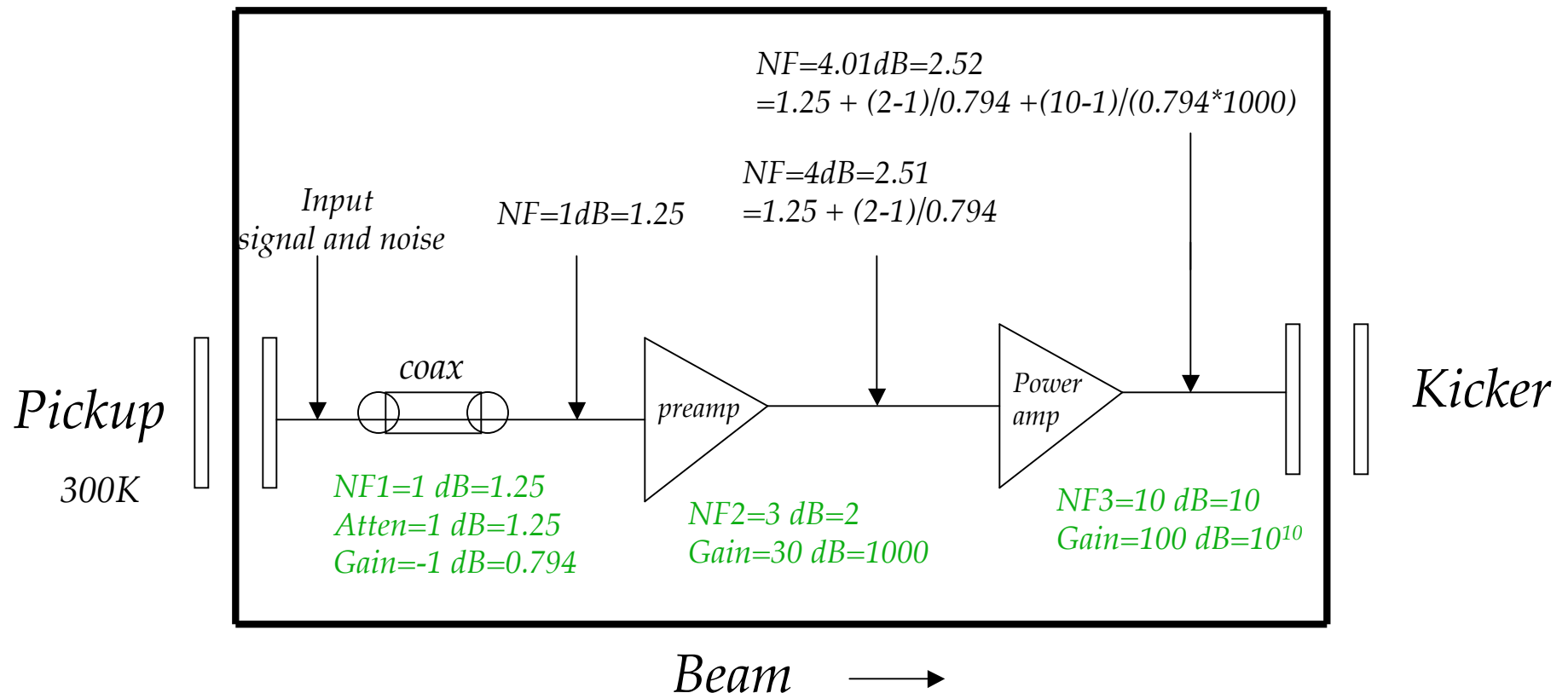




Fermilab

Noise in RF Systems

Typical Stochastic Cooling Feedback System

Case I

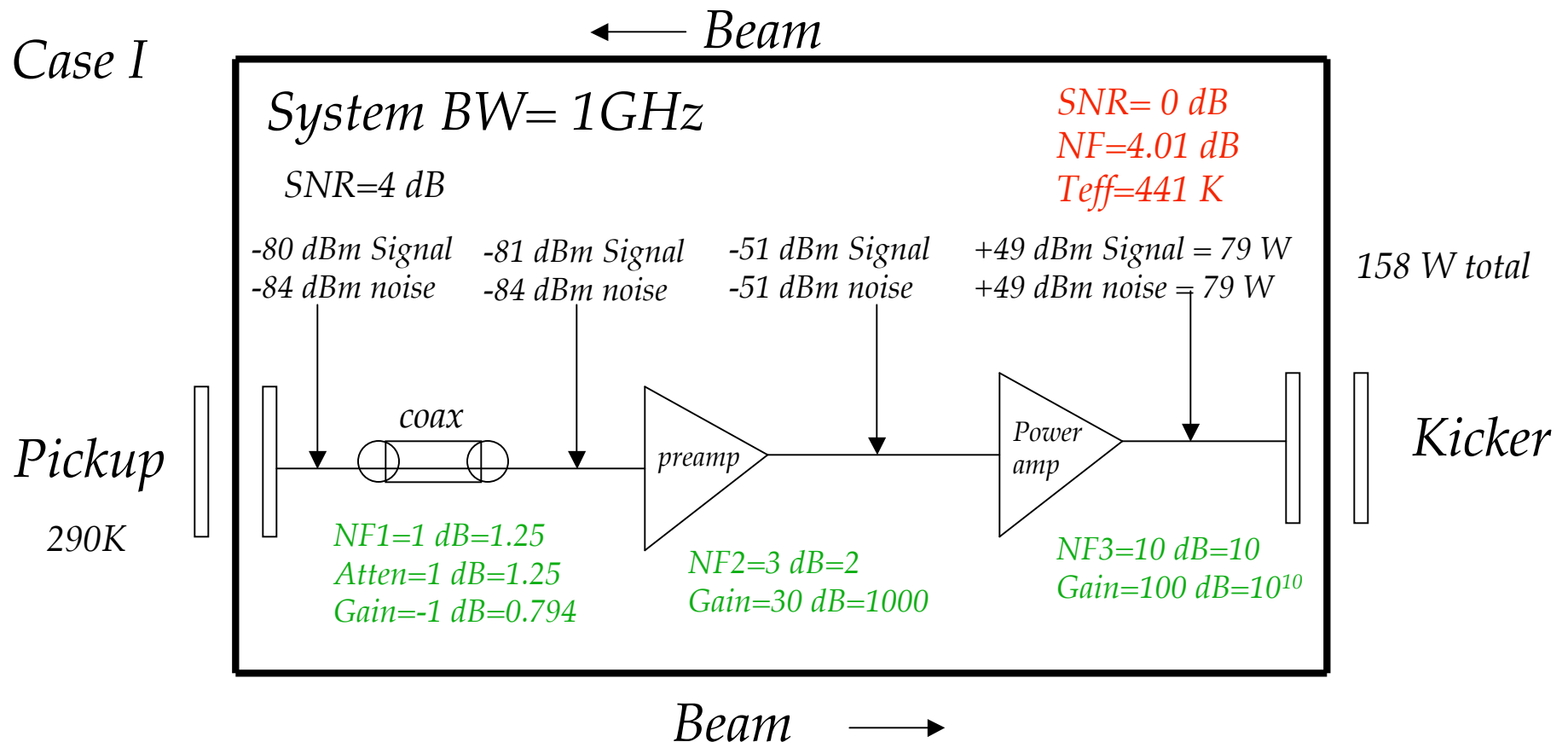



Fermilab

Noise in RF Systems


Typical Stochastic Cooling Feedback System

← Beam

Case II
Buy better
preamp

Pickup

290K

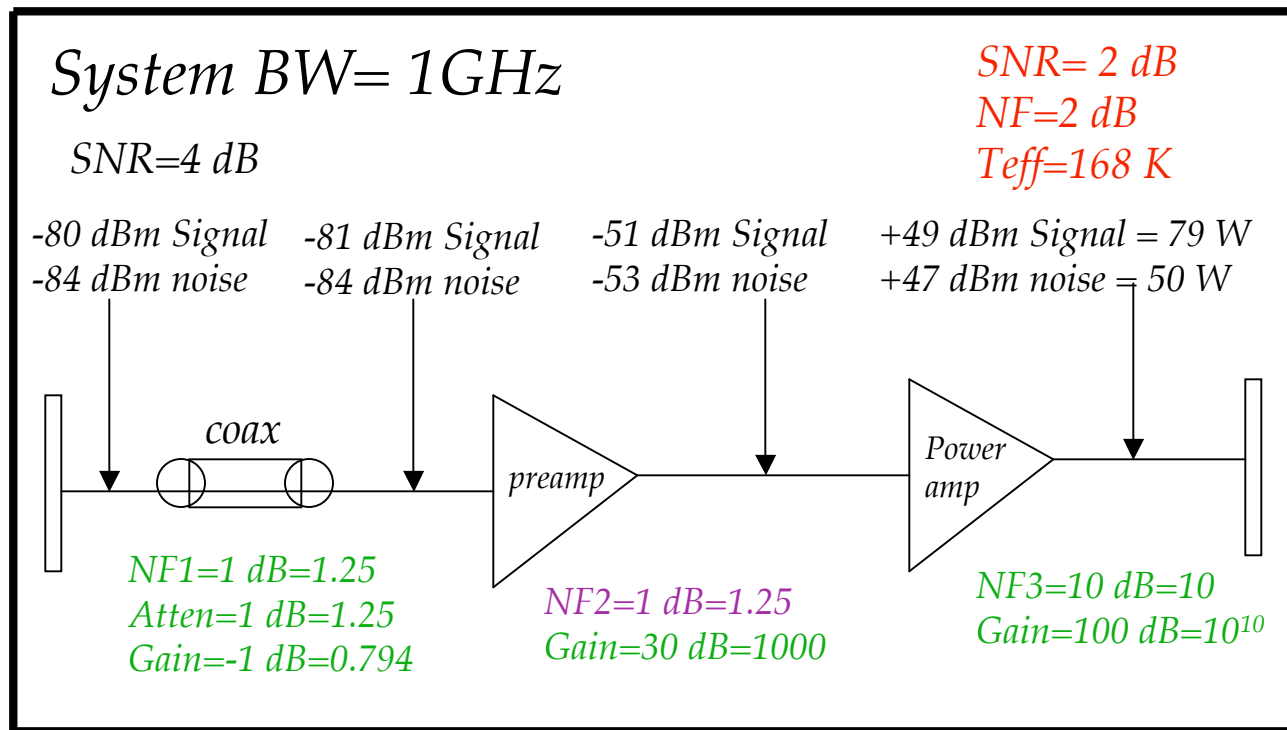

129 W total

Kicker

Beam →



Fermilab

Noise in RF Systems


Typical Stochastic Cooling Feedback System

← Beam

Case III
Buy better
Preamp
& chill
front end

Pickup

80K

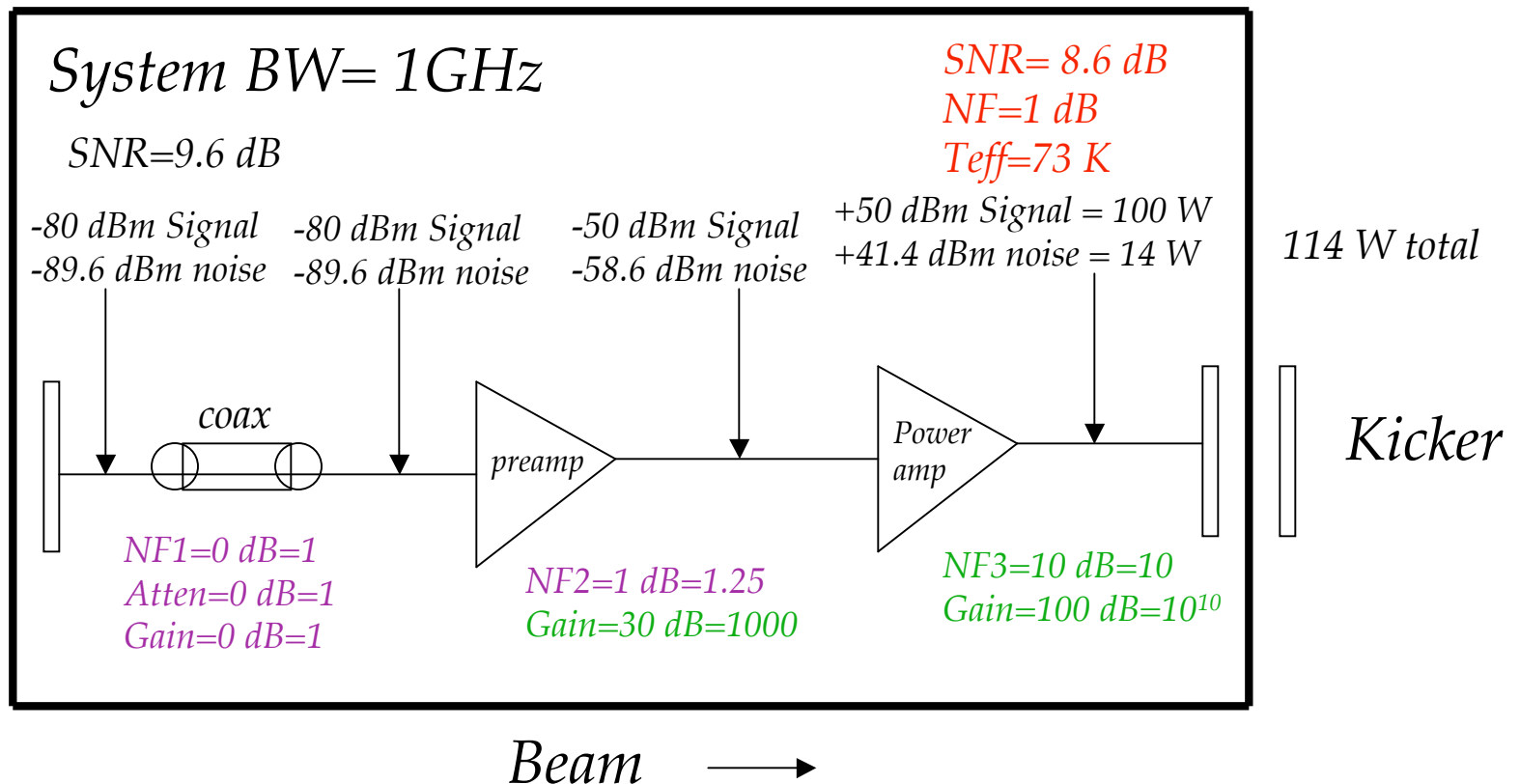



Fermilab

Noise in RF Systems

\$\$ What's the Cost \$\$

Power costs \$100 per watt for this system

Case I: Warm pickup and 3 dB NF preamp

79 watts signal + 79 watts noise = 158 watts

*Did not meet 100 watt signal minimum so must add
26% more total power for 200 Watts*

Preamp cost.....\$500

Power cost.....\$20,000

Subtotal.....\$20,500



Fermilab

Noise in RF Systems

\$\$ What's the Cost \$\$

Power costs \$100 per watt for this system

Case II: Warm pickup and 1 dB NF preamp

79 watts signal + 50 watts noise = 129 watts

*Did not meet 100 watt signal minimum so must add
26% more total power for 162 Watts*

Preamp cost.....\$2000

Power cost.....\$16,200

Subtotal.....\$18,200



Fermilab

Noise in RF Systems

\$\$ What's the Cost \$\$

Power costs \$100 per watt for this system

Case III: Cold pickup and 1 dB NF preamp

100 watts signal + 14 watts noise = 114 watts

Cryogenics\$50,000

Preamp cost.....\$2000

Power cost.....\$11,400


Subtotal.....\$63,400



Fermilab

Noise in RF Systems

Debuncher Stochastic Cooling Cryo Preamp

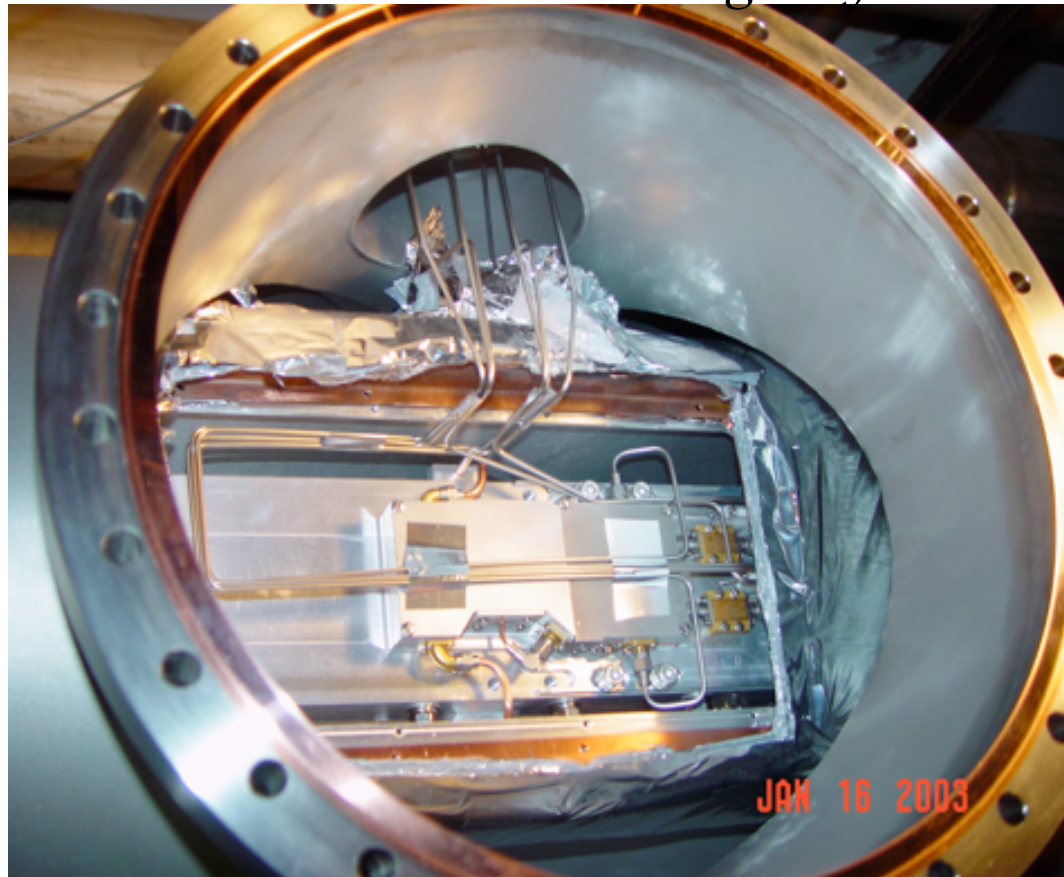

R. J. Pasquinelli



Fermilab

Noise in RF Systems

What if?



Ferrite Saturation?



Power Handling?



*Tight fit?
No room
For
More Kickers*

R. J. Pasquinelli



Fermilab

Noise in RF Systems

Noise Basics

Where is the noise floor?

Temperature Dependent

Noise Energy = kT = joules = watt seconds


$$=(1.38 \times 10^{-23} \text{ joules/K}) \times (290 \text{ K})$$

$$=4 \times 10^{-21} \text{ joules}$$

$$=4 \times 10^{-18} \text{ milliwatt seconds}$$

$$=-174 \text{ dBm per Hz}$$

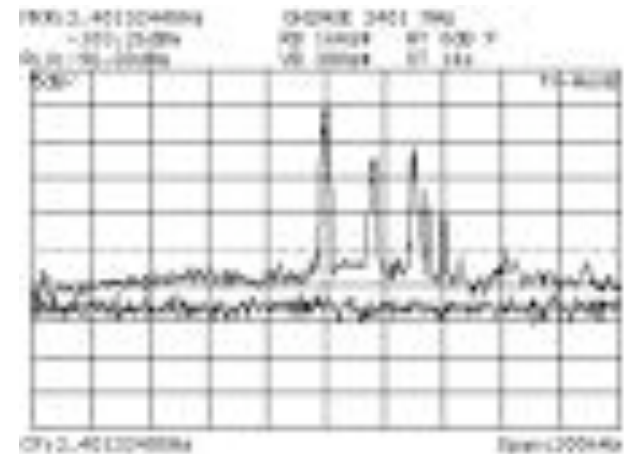Have a MHz of Bandwidth then add 60 dB for -114 dBm per MHz






Fermilab

Noise in RF Systems

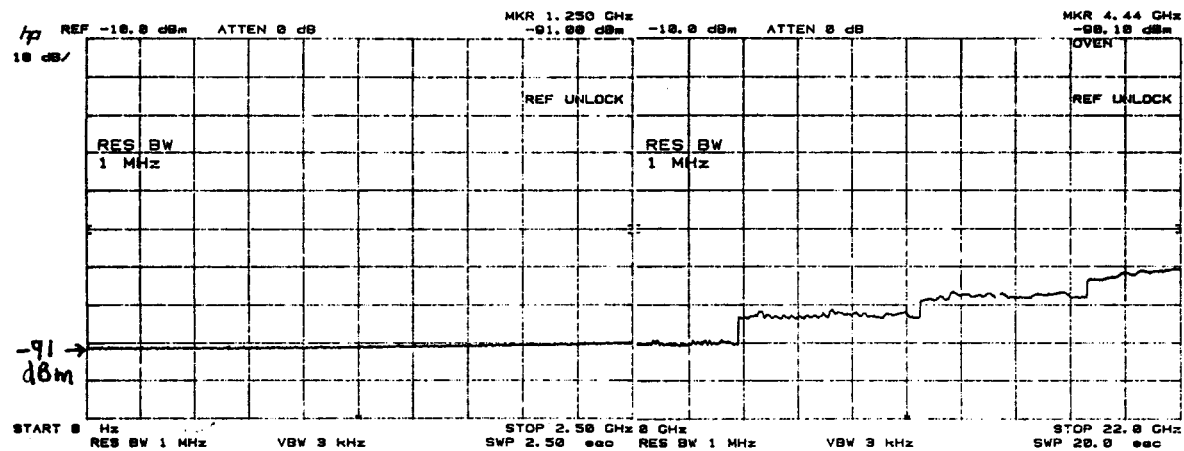Noise Performance of Swept Frequency Spectrum Analyzer




*With a Resolution Bandwidth of 1 MHz noise floor = -91 dBm
Some 23 dB worse than ideal, i.e. $NF = 23$ dB, $T_{eff} = 58,000$ deg K*



Fermilab

Noise in RF Systems

Optical Amplifier Noise Performance

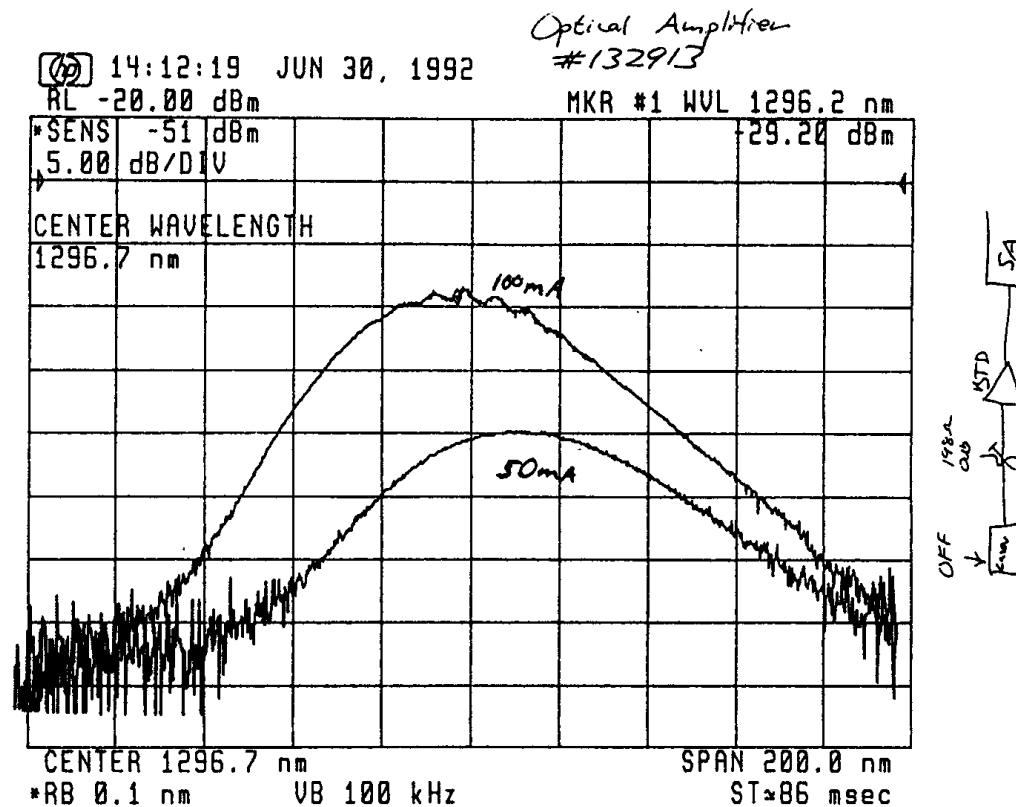


R. J. Pasquinelli



Fermilab

Noise in RF Systems

Synchronous Phase & Phase Stability

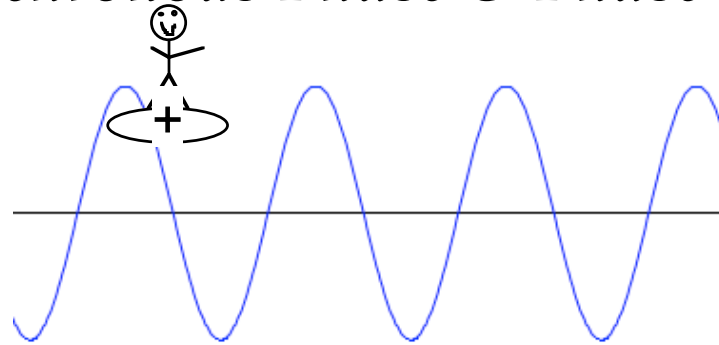


R. J. Pasquinelli




Fermilab

Noise in RF Systems

Plot of Phase Noise vs Frequency

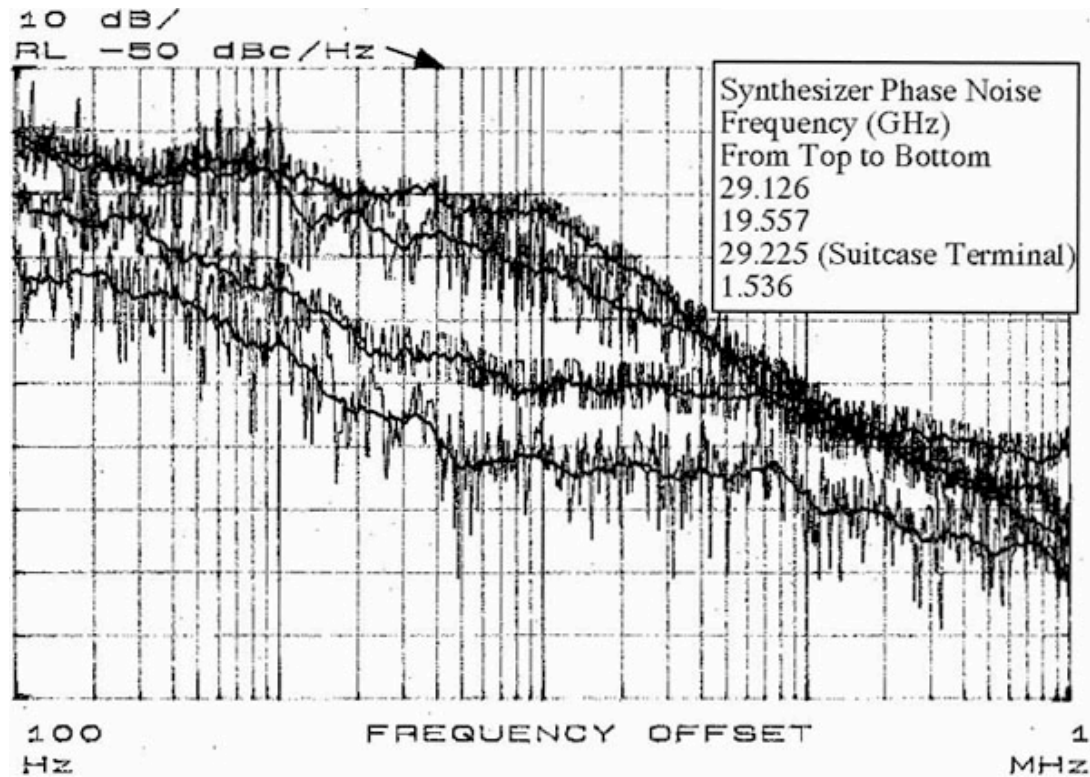


R. J. Pasquinelli

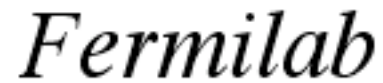

Noise in RF Systems

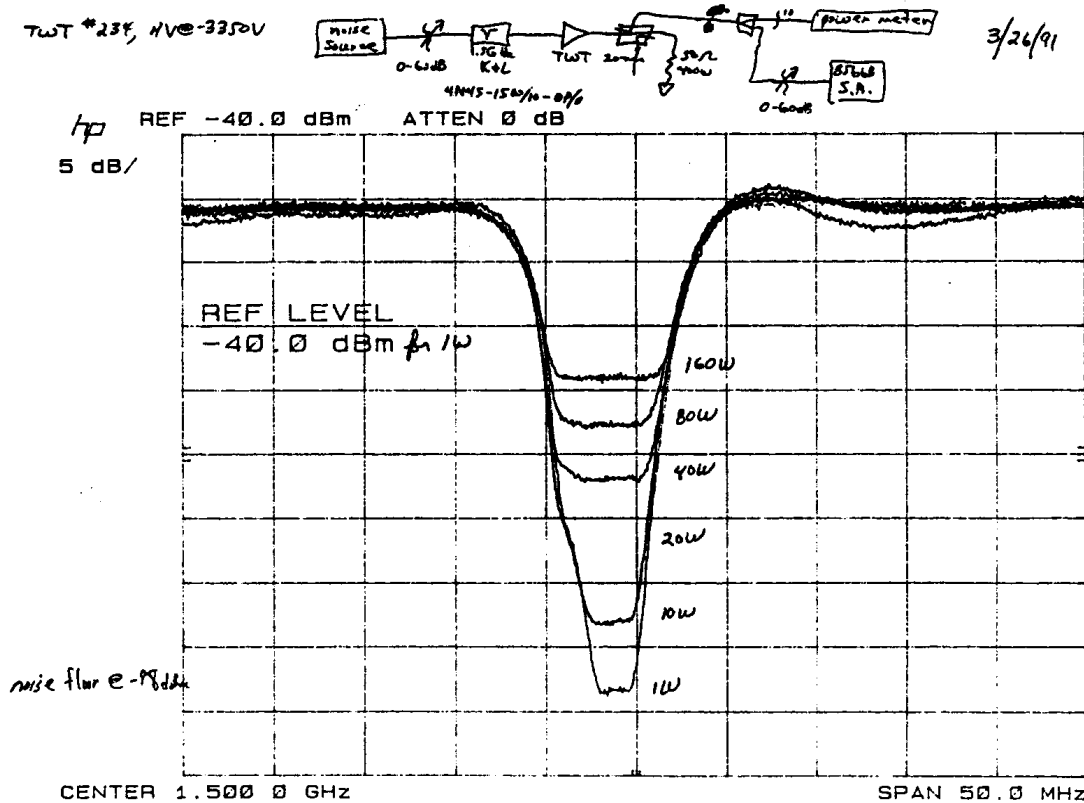Intermodulation Noise in a Power Amplifier






Fermilab

Noise in RF Systems

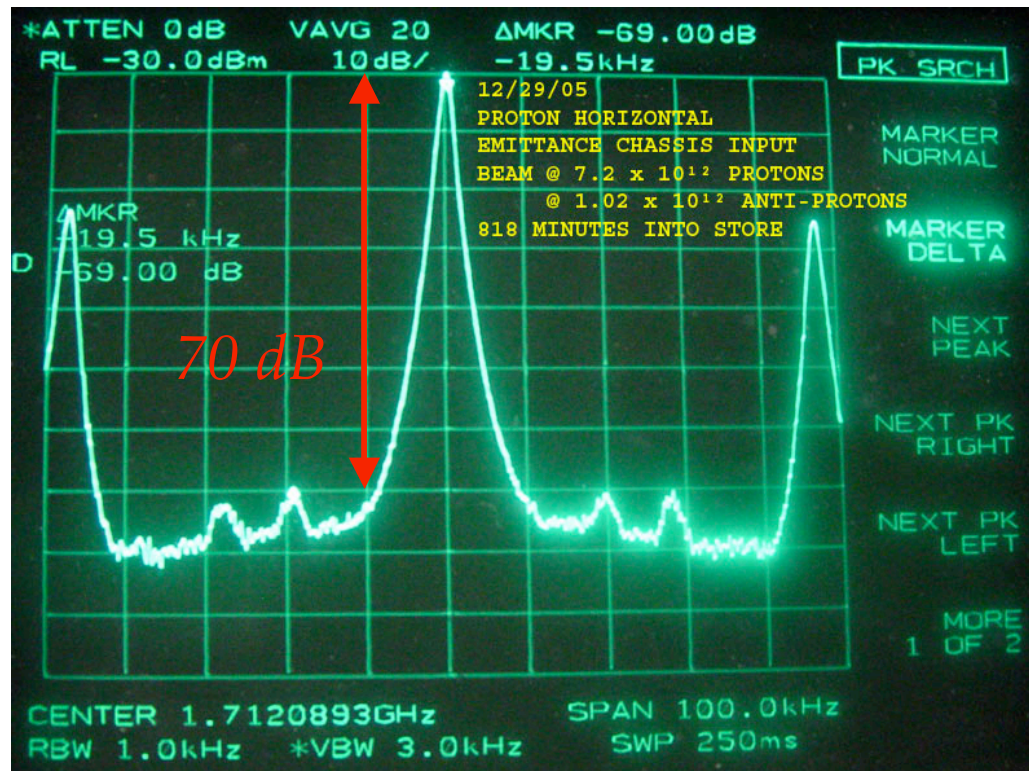Coherent Beam Signal Noise Tevatron Schottky Signal




R. J. Pasquinelli




Fermilab


Noise in RF Systems

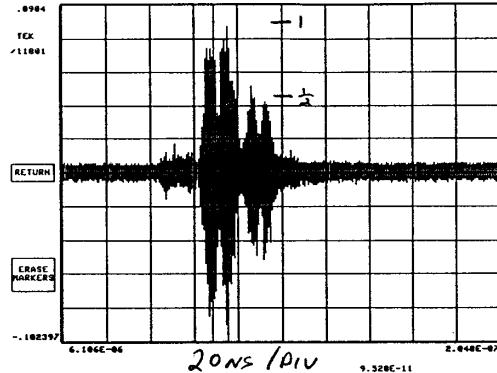

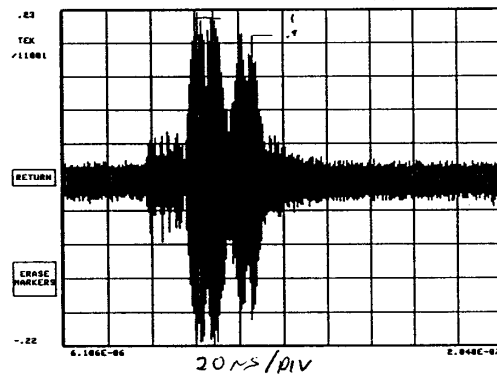Tevatron Schottky Time Domain Signals
After pickup



After pre-amplifier

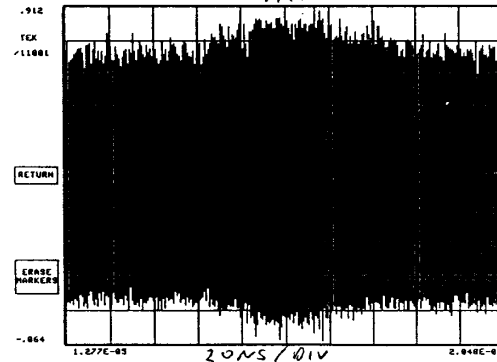

After power amplifier

*Peak Power
Levels can
Saturate the system
But not be
Obvious in the
Frequency Domain*



R. J. Pasquinelli



Fermilab

Noise in RF Systems

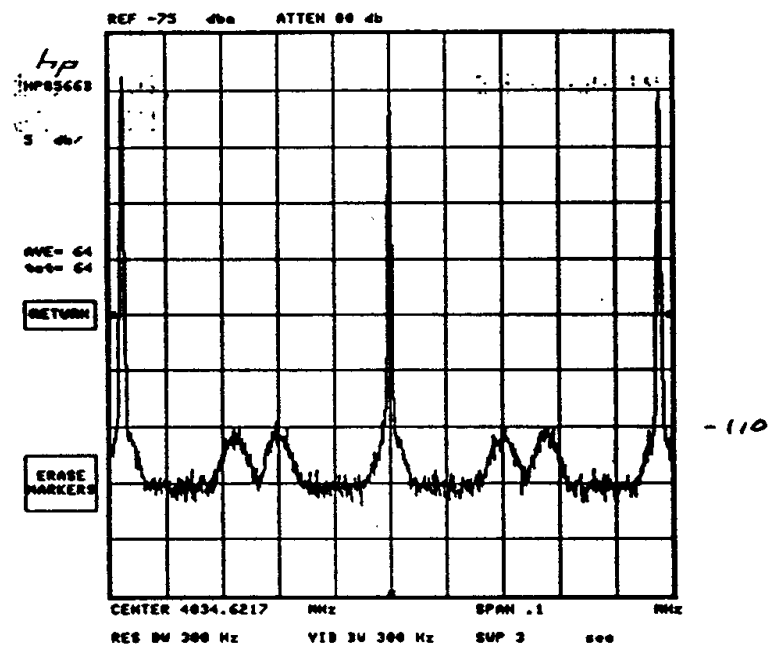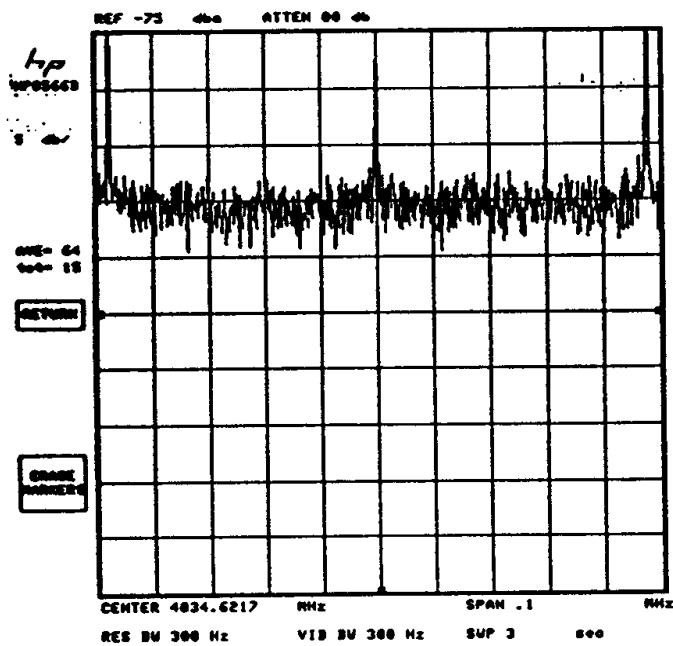Effects by gating on Tevatron Schottky Signal




R. J. Pasquinelli



Fermilab

Noise in RF Systems

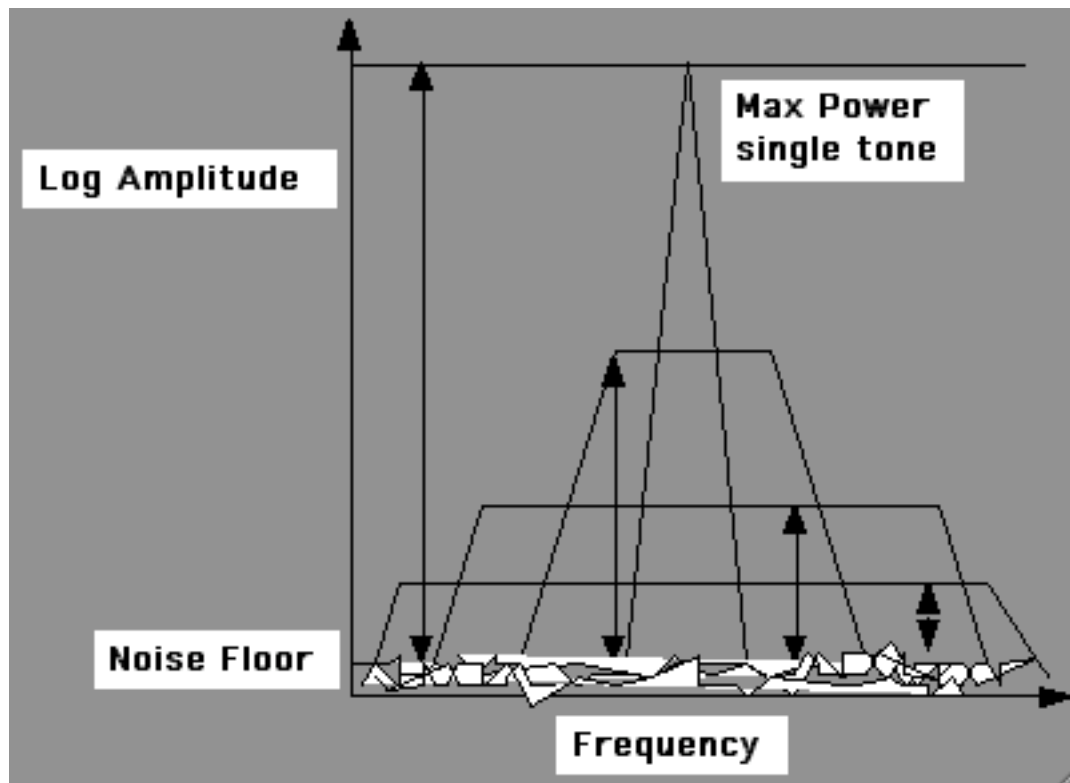Dynamic Range = Max operable power/Noise floor power



*Total Power
Is the
Integral across
Full bandwidth*

R. J. Pasquinelli



Fermilab

Noise in RF Systems

Digital Connection

How many bits?



Digital is base two, so every
Bit is 2 x voltage or 6 dB

Take required dynamic range dB
and
Divide by 6 dB for number of bits!



Fermilab

Noise in RF Systems



R. J. Pasquinelli